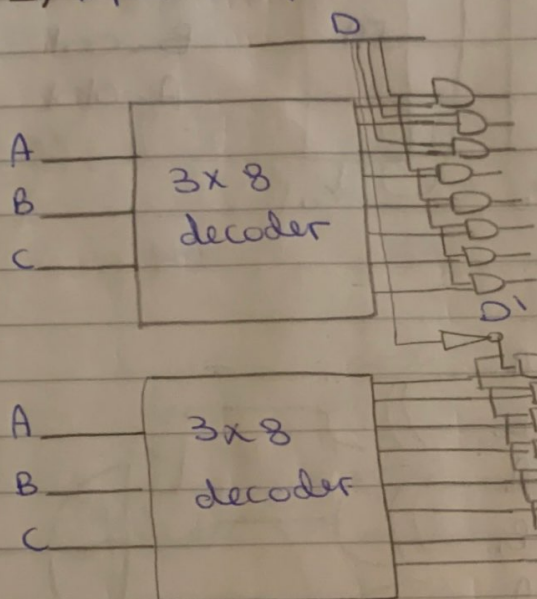


Tutorial 8

Tuesday, December 22, 2020

- * Encoding \rightarrow encryption
- * Decoder \rightarrow n input, 2^n output

1) input: 4 inputs (A, B, C, D)




A	B	C	D
0	0	0	0
0	0	0	1

different


1	0
1	1
0	0
0	1
1	0
1	1

* By default enable is 1

2)

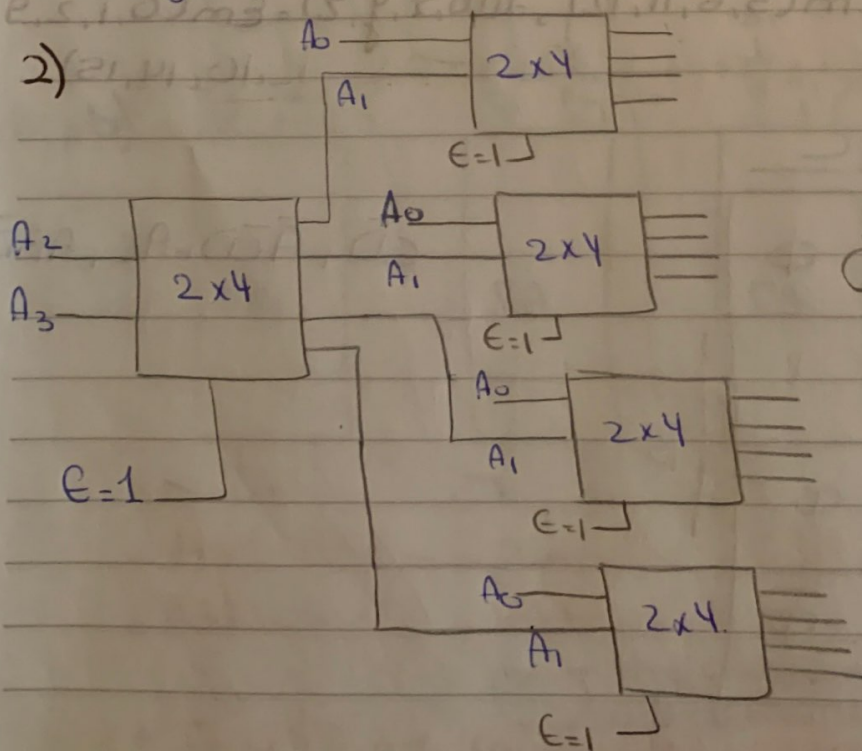

Logism (label for labeling hehe!)

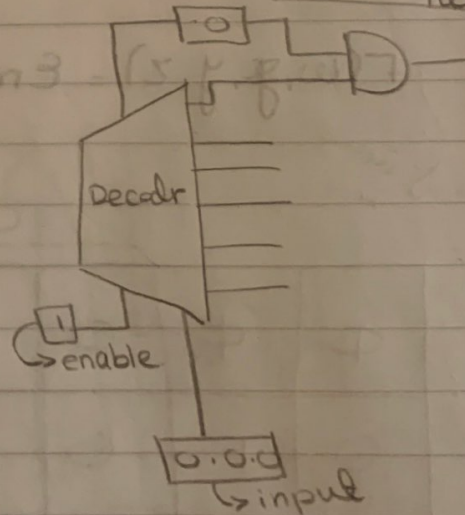


* If E is 0, no output


A₃ A₂ A₁ A₀
Selectors

2's complement
 [x x]
 → no output 2 bits

3) a)

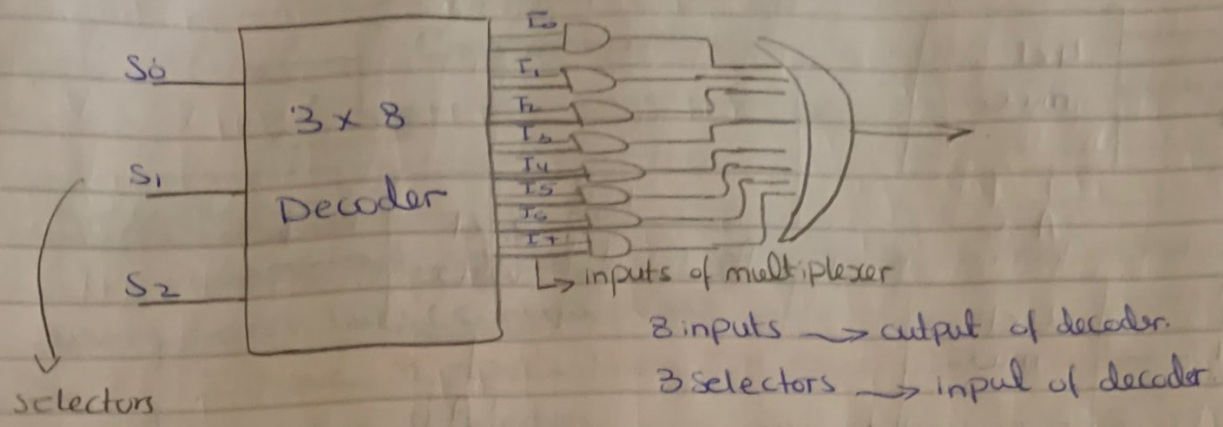


b)

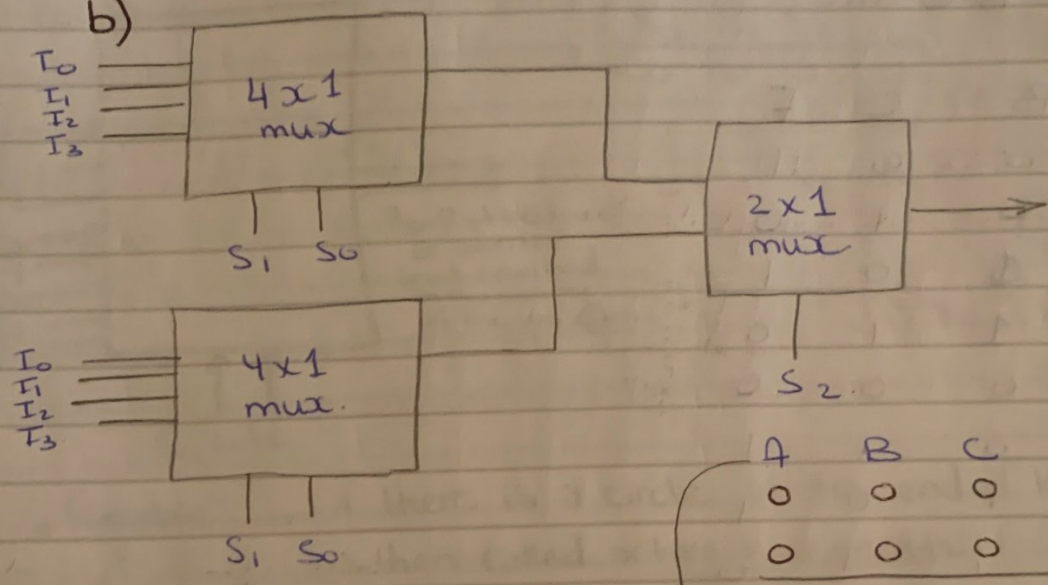

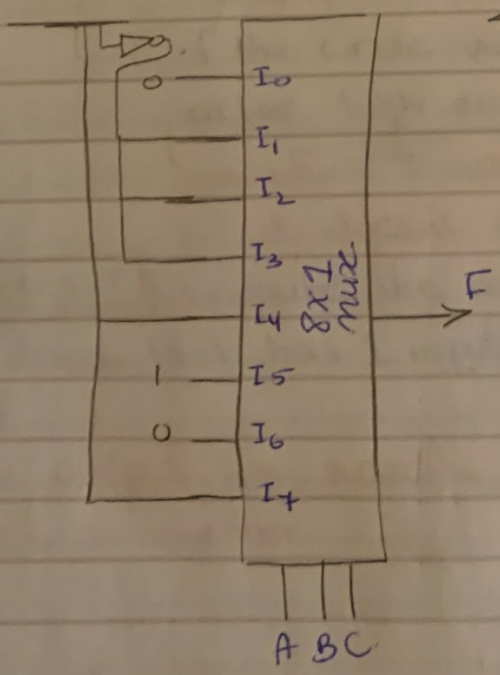
4)

Truth table & Diagram are the answer together



A	B	C	D	F	input
0	0	0	0	0	0
0	0	0	1	0	
0	0	1	0	1	D'
0	0	1	1	0	
0	1	0	0	1	D'
0	1	0	1	0	
0	1	1	0	1	D'
0	1	1	1	0	
1	0	0	0	0	D
1	0	0	1	1	
1	0	1	0	1	1
1	0	1	1	1	
1	1	0	0	0	0
1	1	0	1	0	
1	1	1	0	0	D
1	1	1	1	1	

6)

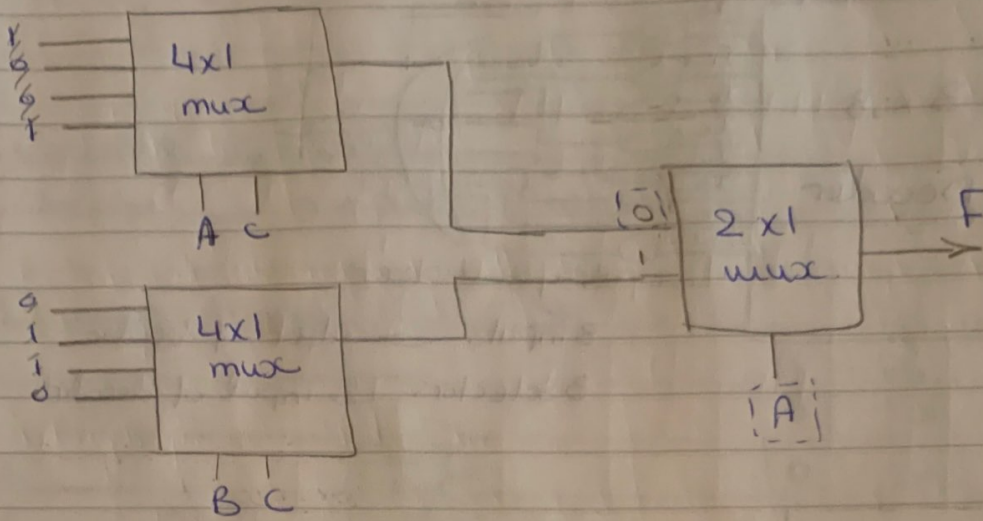

A	B	C	F
0	0	0	1
0	0	1	0
0	0	0	1
0	1	1	0
1	0	0	0
1	0	1	1
0	1	0	1
0	1	1	0

1	0	1	0
0	1	1	0
1	0	0	1
0	1	0	1
1	0	1	0
0	1	1	0
0	0	0	1
1	1	0	1
1	0	1	0
1	1	1	0
0	0	0	1
0	1	0	1
0	0	1	1
1	1	1	1